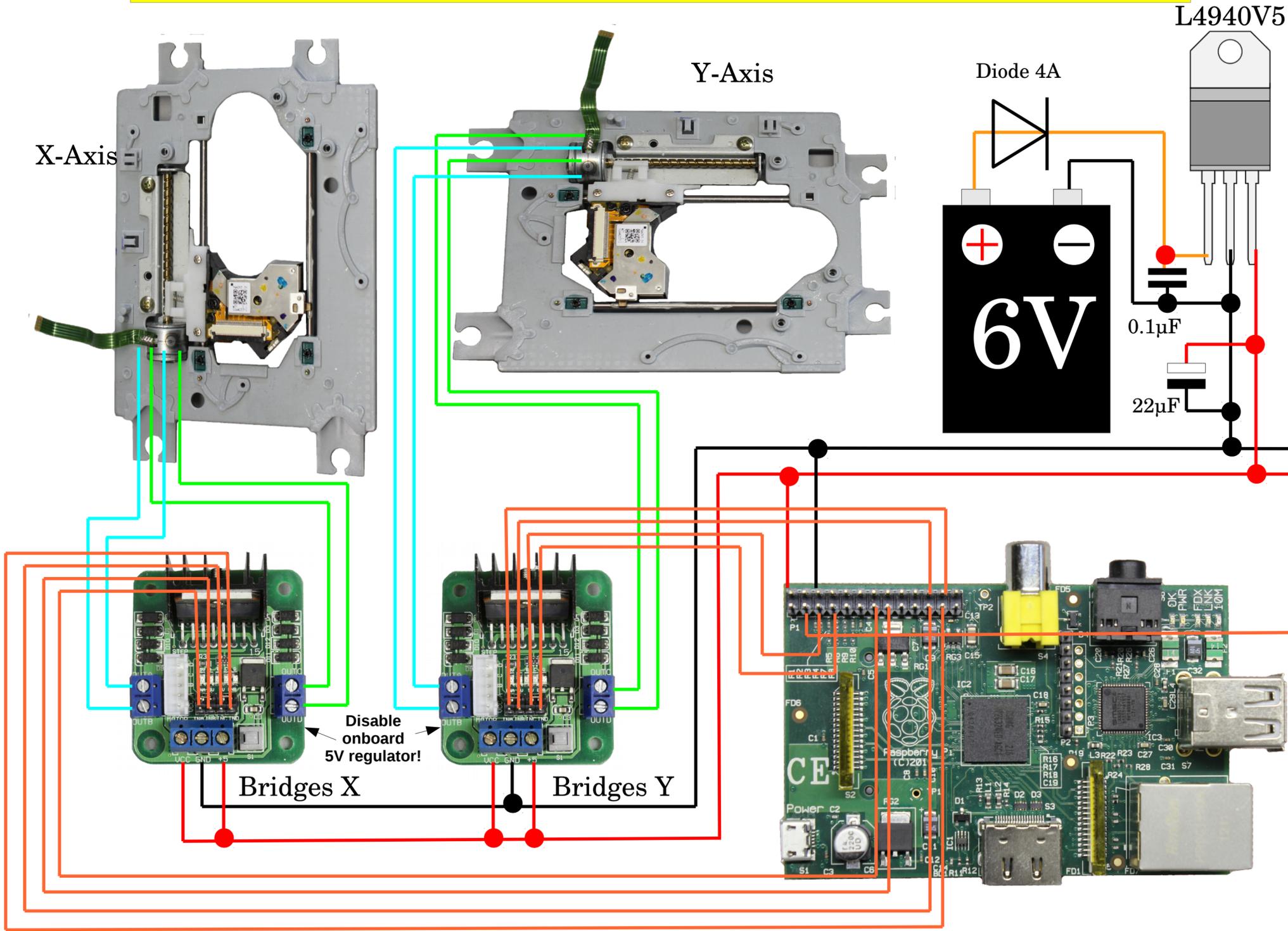


# Plotter CDRom V 0.6

Source & info: [www.HomoFaciens.de](http://www.HomoFaciens.de)

Use the pin header numbers (P1-xx) for wiring up your plotter, no matter what Raspberry Pi version you have!



## Bridges X:

- InA to GPIO 2 = P1-13
- InB to GPIO 3 = P1-15
- InC to GPIO 13 = P1-21
- InD to GPIO 14 = P1-23

- Out A + Out B to stepper motor X coil 1
- Out C + Out D to stepper motor X coil 2

Connect +5V AND Vcc (sometimes marked +12V) of the L298N to the +5V line of the output of the voltage regulator!


Ground to minus of battery.

There is usually a 5V regulator on the L298N boards that can be enabled/disabled by a switch or a jumper.

**Disable that onboard voltage regulator!**
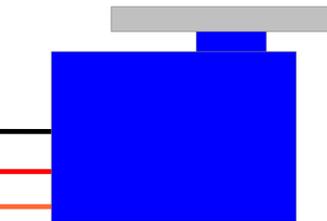
## Servo:

Control line (Orange or white to GPIO 8 = P1-3)



Servo

## Bridges Y:

- InA to GPIO 10 = P1-24
- InB to GPIO 6 = P1-22
- InC to GPIO 9 = P1-5
- InD to GPIO 7 = P1-7

- Out A + Out B to stepper motor Y coil 1
- Out C + Out D to stepper motor Y coil 2

Connect +5V AND Vcc (sometimes marked +12V) of the L298N to the +5V line of the output of the voltage regulator!

Ground to minus of battery